 


# FIR Filter

## ■ 3 TAP FIR filter



1-1

- This architecture represents the direct-form implementation of a 3-tap Finite Impulse Response filter. The number of “taps” is equal to the number of multiplications.
- A history of the input sample,  $X$ , is captured and feeds a merged sum of products circuit where each data sample is multiplied by a corresponding coefficient,  $C0$ ,  $C1$ ,  $C2$ .
- This type of architecture is used for high sample rate filters. It provides high sample rate because it computes the sum of all products in parallel.
- For lower sample rate filters fewer multipliers can be used. A multiplier-accumulate type architecture can be used if the sample rate is low enough (one multiplication per clock cycle).

## ■ FIR Filter

- Works With Any Width/Format Coeff and Data
- Works With Any Number of Taps

```
function FIR (Z,X,repl(i,fnArgs()-2,"") {C{i}});  
  integer taps=fnArgs()-2;  
  input X,repl(i,taps,"") {C{i}};  
  wire XX,repl(i,taps,"") {X{i}};  
  XX = sreg(X,taps-1,repl(i,taps,"") {X{i}});  
  output Z = repl(i,taps,"+") {X{i}*C{i}};  
endfunction
```

```
X=FIR(D1,C0,256,C2);      // 3-tap, some constant coeffs  
Y=FIR(A,C0,C1,C2,C3);    // 4-taps  
Z=FIR(D1,-5,10,-5);      // 3-taps all constant coeffs  
// Note:      func(Z,A);  
// and        Z=func(A);  
// are equivalent. And fnArgs() is 2 in both cases.
```

1-2

- MCL is a very powerful language. It is very flexible and allows for significant parameterization. This enables very high levels of design reuse.
- The FIR() function above describes a high sample-rate FIR filter that can be re-used for any number of taps and any width/format for the data and coefficients.
  - Input, X, can be any width, signed/unsigned
  - Coefficients can be variable, constant, any width, signed/unsigned
  - Number of taps is determined automatically with the fnArgs() function
  - All of these IO characteristics are determined based on the function call to FIR()
- MC will automatically synthesize Canonical Signed-Digit multipliers for any constant coefficient multiplier.
  - This does not rely on gate level optimization which would not produce the best results
  - If the constant happens to be a power of 2, there will be only one partial product. This is simply a degenerate case of a CSD multiplier.